

ELC 2137 Lab 08: 4-digit Display

Yiting Wang

October 21, 2020

Summary

Type the summary of your experiment and results here.

Q&A

There is no question in the lab 08 assignment.

Results

Figure 1 is the simulation waveform and ERT of the mux2.

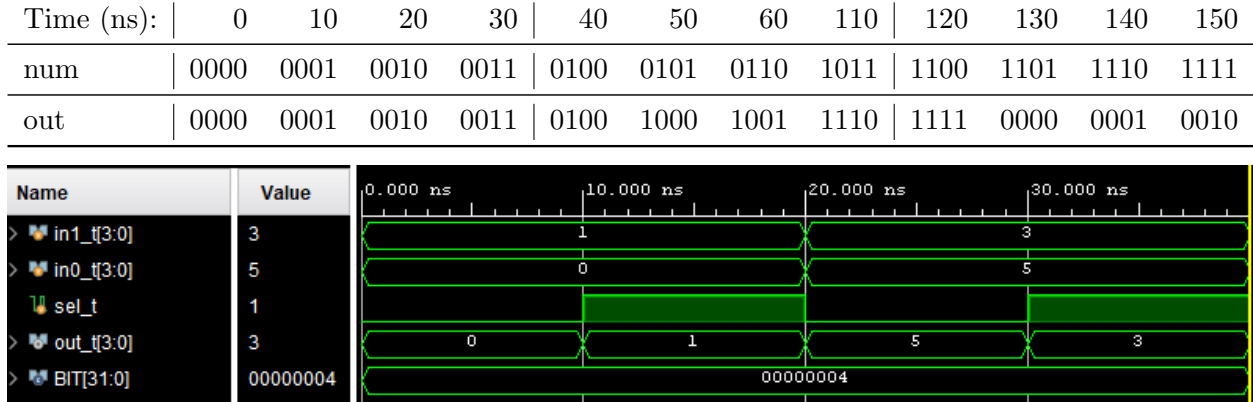


Figure 1: the simulation waveform and ERT of the mux2

Figure 2 is the simulation waveform and ERT of the mux4.

.

Figure 3 is the simulation waveform and ERT of the anode decoder.

.

Time (ns):	0	10	20	600	610	620	630
Bin	000000	000001	000010	111100	111101	111110	111111
ones	0000	0001	0010	0000	0001	0010	0011
tens	0000	0000	0000	0110	0110	0110	0110

 


Figure 2: the simulation waveform and ERT of the mux4

Time (ns):	0	10	20	30	40	50	20430	20440	20450	20460
Bin	000	001	002	003	004	005	7fb	7fc	7fd	7fe
ones	0000	0001	0010	0011	0100	0101	0011	0100	0101	0110
tens	0000	0000	0000	0000	0000	0000	0100	0100	0100	0100
hund	0000	0000	0000	0000	0000	0000	0000	0000	0000	0000
thou	0000	0000	0000	0000	0000	0000	0010	0010	0010	0010

 


Figure 3: the simulation waveform and ERT of the anode decoder

Code

File Inclusion

Listing 1: mux2 Verilog code

```
'timescale 1ns / 1ps
//
// //////////////////////////////////////
// Company: ELC 2137
// Engineer: Yiting Wang
// Create Date: 10/15/2020
//
// //////////////////////////////////////

module mux2
    #(parameter BIT=4)
```

```

(
    input [BIT-1:0] in1,
    input [BIT-1:0] in0,
    input sel,
    output [BIT-1:0] out
);

    assign out = sel ? in1 : in0;

endmodule

```

File Inclusion

Listing 2: mux2 Test Benches Verilog code

```

`timescale 1ns / 1ps
//
// //////////////////////////////////////
// Company: ELC 2137
// Engineer: Yiting Wang
// Create Date: 10/15/2020
//
// //////////////////////////////////////

module mux2_test();
localparam BIT=4;
    reg [BIT-1:0] in1_t, in0_t;
    reg sel_t;
    wire [BIT-1:0] out_t;

    mux2 dut(
        .in1(in1_t),
        .in0(in0_t),
        .sel(sel_t),
        .out(out_t)
    );

    initial begin
        in1_t = 16'h1111; in0_t = 16'h0000; sel_t = 0; #10;
        sel_t = 1; #10;
        in1_t = 16'h1013; in0_t = 16'h0105; sel_t = 0; #10;
        sel_t = 1; #10;
        $finish;
    end

endmodule

```

File Inclusion

Listing 3: mux4 Verilog code

```

`timescale 1ns / 1ps
//
//
// Company: ELC 2137
// Engineer: Yiting Wang
// Create Date: 10/15/2020
//
//

module mux4
    #(parameter BIT=4)
    (
        input [BIT-1:0] in3, in2, in1, in0,
        input [1:0] sel,
        output reg [BIT-1:0] out
    );

    always @*
        case(sel)
            2'b11: out = in3;
            2'b10: out = in2;
            2'b01: out = in1;
            default: out = in0;
        endcase
endmodule

```

File Inclusion

Listing 4: mux4 Test Benches Verilog code

```

`timescale 1ns / 1ps
//
//
// Company: ELC 2137
// Engineer: Yiting Wang
// Create Date: 10/15/2020
//
//

module mux4_test();
    localparam BIT=4;
    reg [BIT-1:0] in3_t, in2_t, in1_t, in0_t;
    reg [1:0] sel_t;
    wire [BIT-1:0] out_t;

    mux4 dut(
        .in3(in3_t), .in2(in2_t), .in1(in1_t), .in0(in0_t),

```

```

        .sel(sel_t),
        .out(out_t)
    );

    integer i;

    initial begin
        in3_t = 16'h1111; in2_t = 16'h0000; in1_t = 16'h1013; in0_t = 16'
            h0105;
        for (i=0; i<=8'h3; i=i+1) begin
            sel_t = i;
            #10;
        end
        $finish;
    end

endmodule

```

File Inclusion

Listing 5: anode decoder Verilog code

```

`timescale 1ns / 1ps
//
// //////////////////////////////////////
// Company: ELC 2137
// Engineer: Yiting Wang
// Create Date: 10/15/2020
//
// //////////////////////////////////////

module anode_decoder(
    input [1:0] in,
    output reg [3:0] out
);

    always @*
        case(in)
            2'b11: out = 4'b0111;
            2'b10: out = 4'b1011;
            2'b01: out = 4'b1101;
            default: out = 4'b1110;
        endcase

endmodule

```

File Inclusion

Listing 6: anode decoder Test Benches Verilog code

```

`timescale 1ns / 1ps

```

```
//
// //////////////////////////////////////
// Company: ELC 2137
// Engineer: Yiting Wang
// Create Date: 10/15/2020
//
// //////////////////////////////////////

module anode_decoder_test();

    reg [1:0] in_t;
    wire [3:0] out_t;

    anode_decoder dut(
        .in(in_t),
        .out(out_t)
    );

    integer i;

    initial begin
        for (i=0; i<=8'h3; i=i+1) begin
            in_t = i;
            #10;
        end
        $finish;
    end

endmodule
```

File Inclusion

Listing 7: sseg4 Verilog code

```
'timescale 1ns / 1ps
//
// //////////////////////////////////////
// Company: ELC 2137
// Engineer: Yiting Wang
// Create Date: 10/15/2020
//
// //////////////////////////////////////

module sseg4(
    input [15:0] data,
    input hex_dec,
    input sign,
    input [1:0] digit_sel,
```

```

input clk,

output reg [6:0] seg,
output dp,
output reg [3:0] an
);

wire [15:0] out_bcd11, out_mux2;
wire [3:0] out_mux4;
wire [6:0] out_sseg_decoder;

bcd11 dut0(
    .in(data[10:0]),
    .ones(out_bcd11[3:0]), .tens(out_bcd11[7:4]), .hund(out_bcd11
        [11:8]), .thou(out_bcd11[15:12])
);

mux2 dut1(
    .in1(data), .in0(out_bcd11), .sel(hex_dec),
    .out(out_mux2)
);

mux4 dut2(
    .in3(out_mux2[15:12]),
    .in2(out_mux2[11:8]),
    .in1(out_mux2[7:4]),
    .in0(out_mux2[3:0]),
    .sel(digit_sel),
    .out(out_mux4)
);

sseg_decoder dut3(
    .num(out_mux4),
    .sseg(out_sseg_decoder)
);

anode_decoder dut4(
    .in(digit_sel),
    .out(an)
);

wire nan;
assign nan = ~an[3];

wire sel_mux2;
assign sel_mux2 = sign & nan;

mux2 dut5(
    .in1(7'b0111111), .in0(out_sseg_decoder), .sel(sel_mux2),
    .out(seg)
);

```

```
        assign dp = 1;
        assign clk = 1;

endmodule
```

File Inclusion

Listing 8: sseg4 manual Verilog code

```
'timescale 1ns / 1ps
//
// //////////////////////////////////////
//
// Company: ELC 2137
// Engineer: Yiting Wang
// Create Date: 10/15/2020
//
// //////////////////////////////////////

module sseg4_manual(
    input [15:0] sw,
    input clk,

    output [6:0] seg,
    output dp,
    output [3:0] an
);

    sseg4 my_sseg(
        .data({ 4'b0000, sw[11:0] }), .hex_dec(sw[15]), .sign(sw[14]), .
        digit_sel(sw[13:12]), .clk(clk),
        .seg(seg), .dp(dp), .an(an)
    );

endmodule
```
