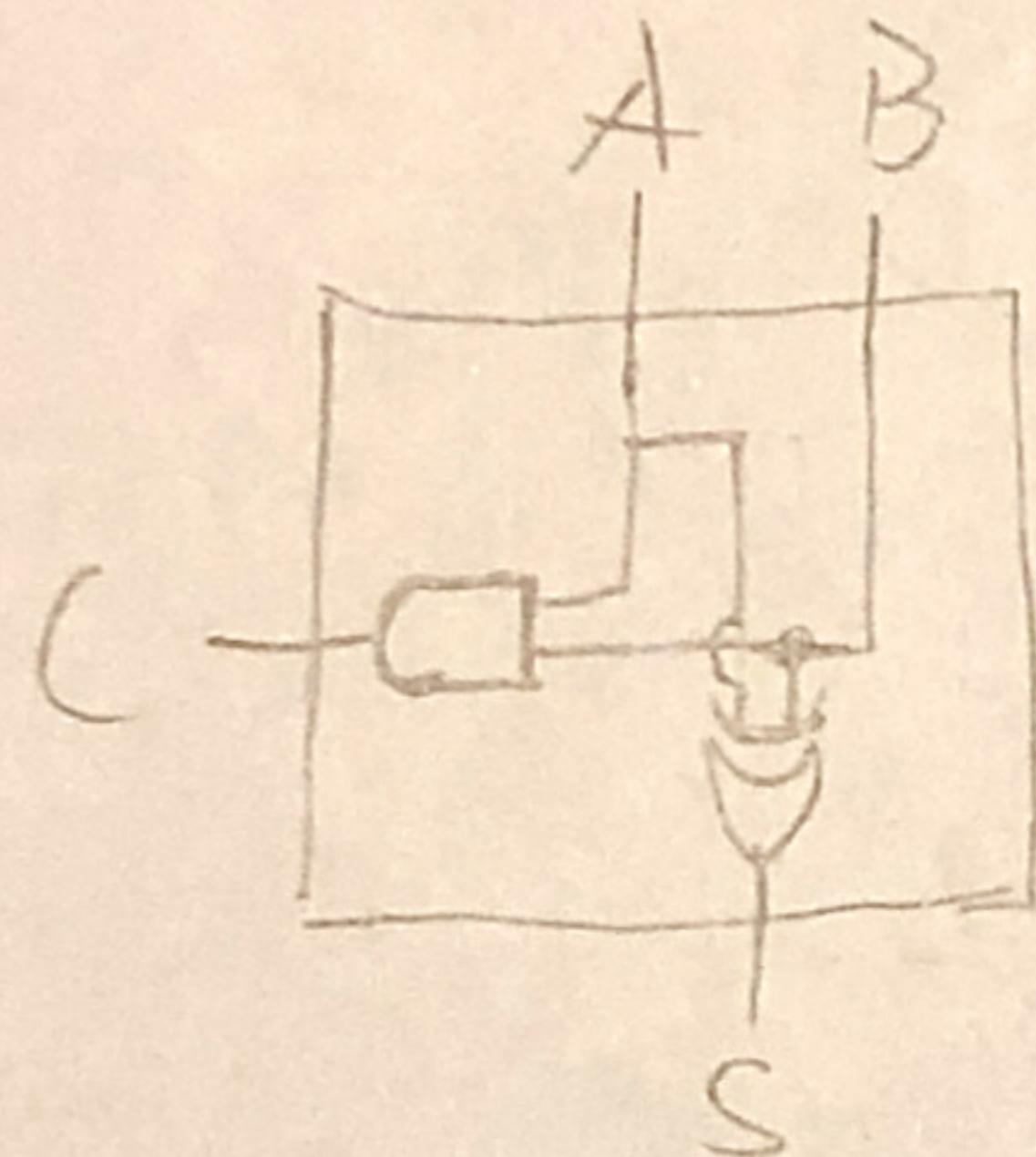
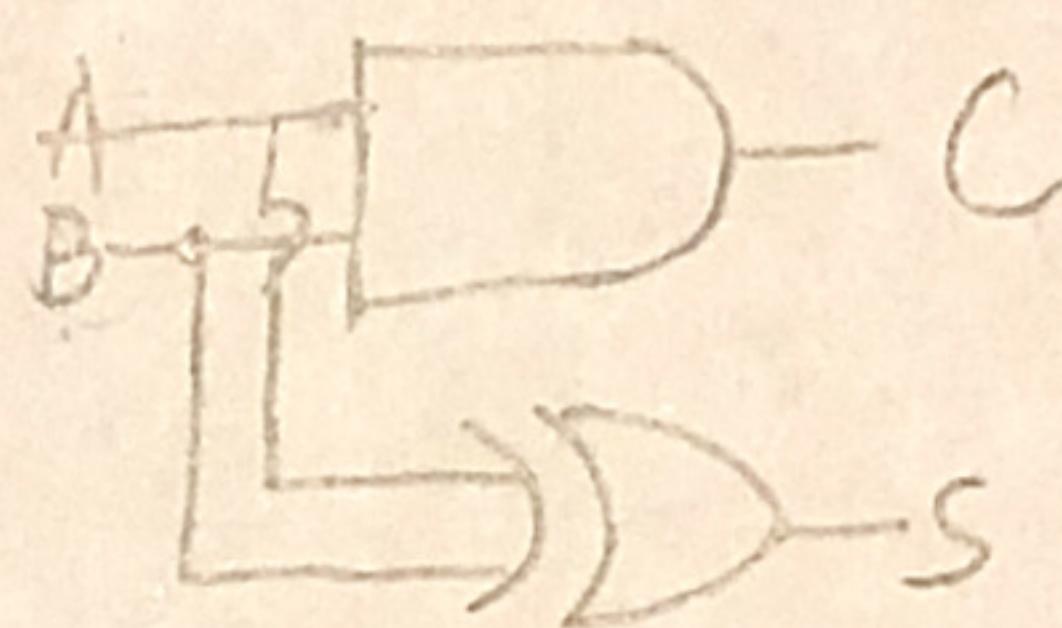
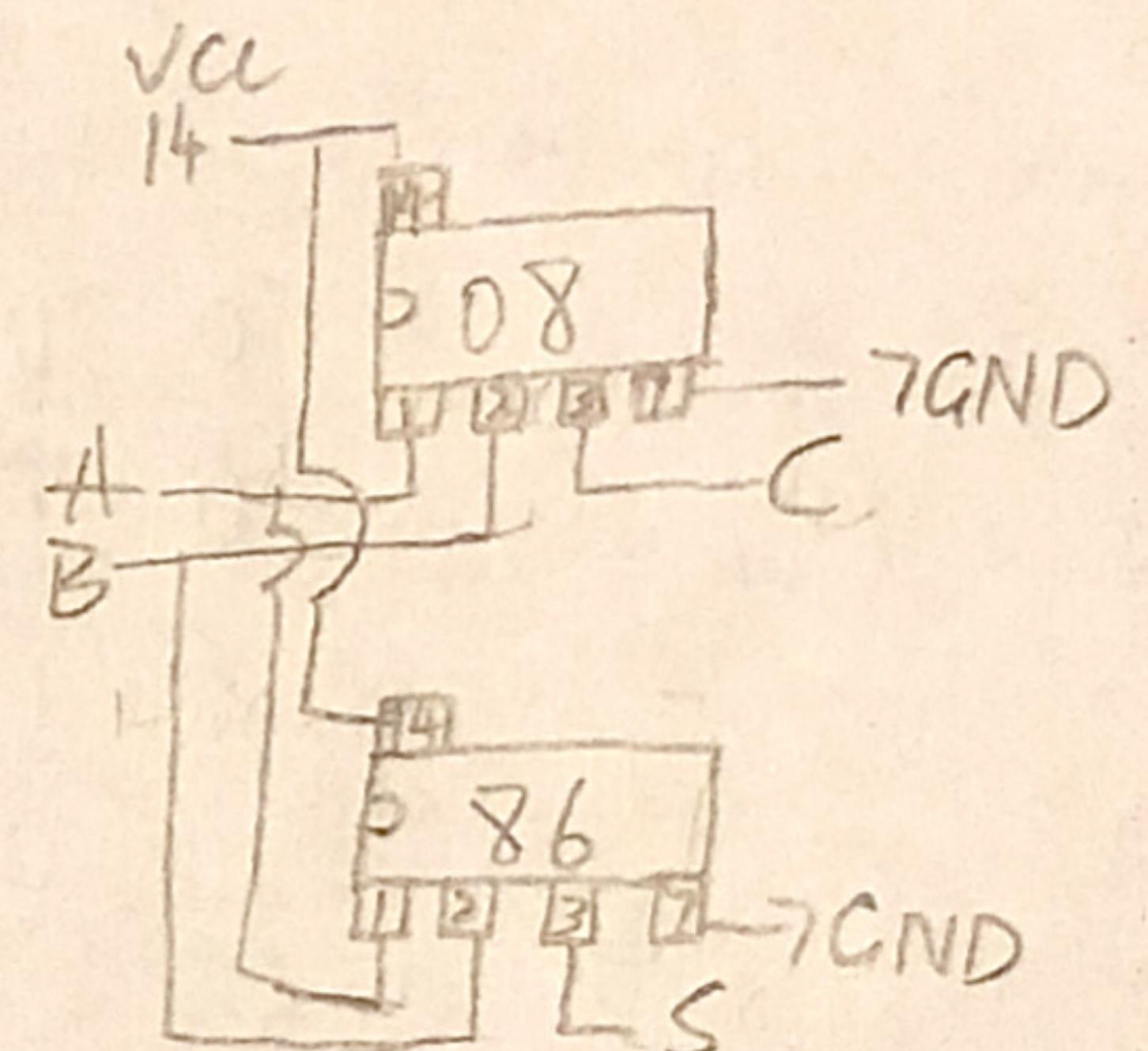
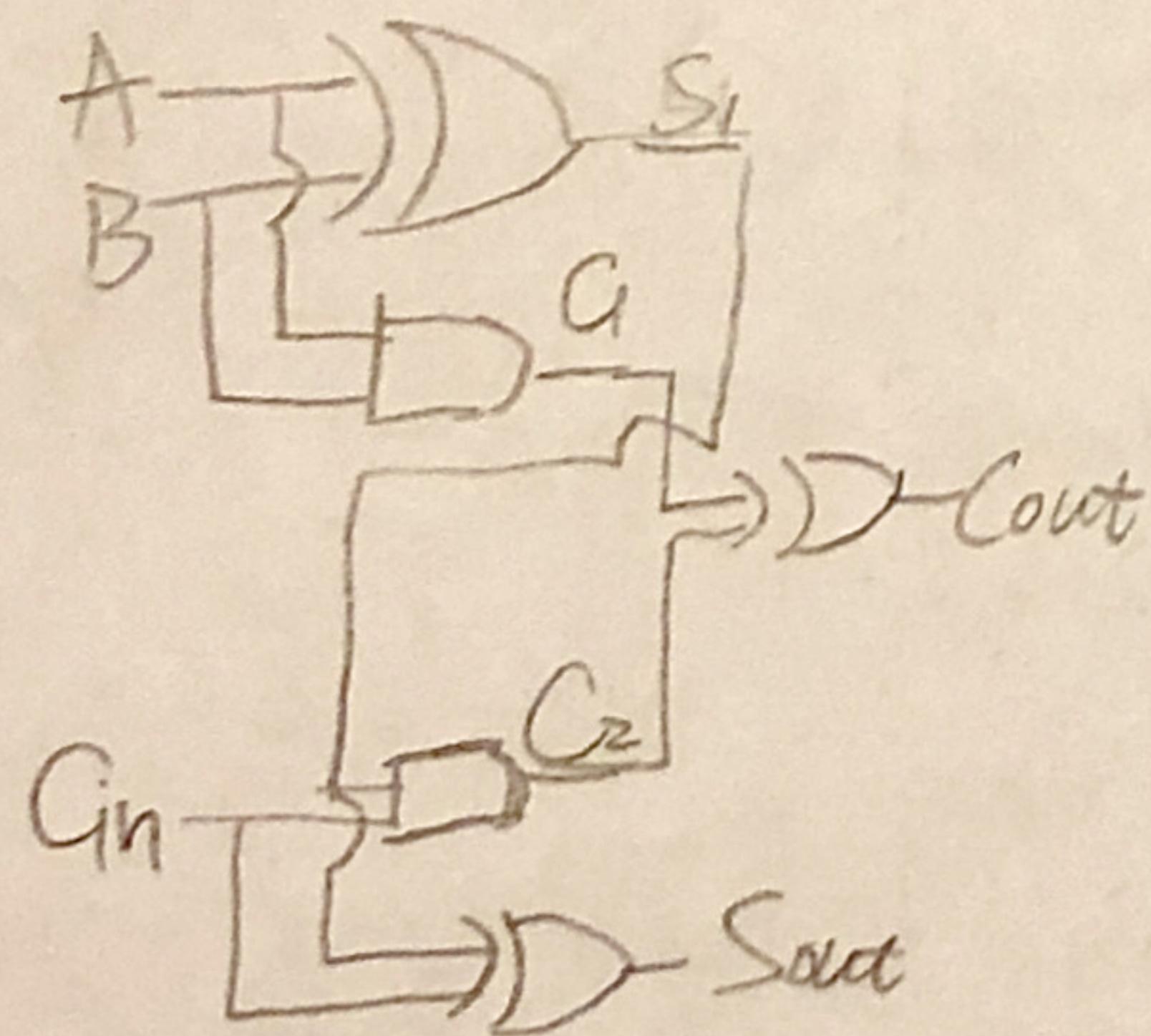
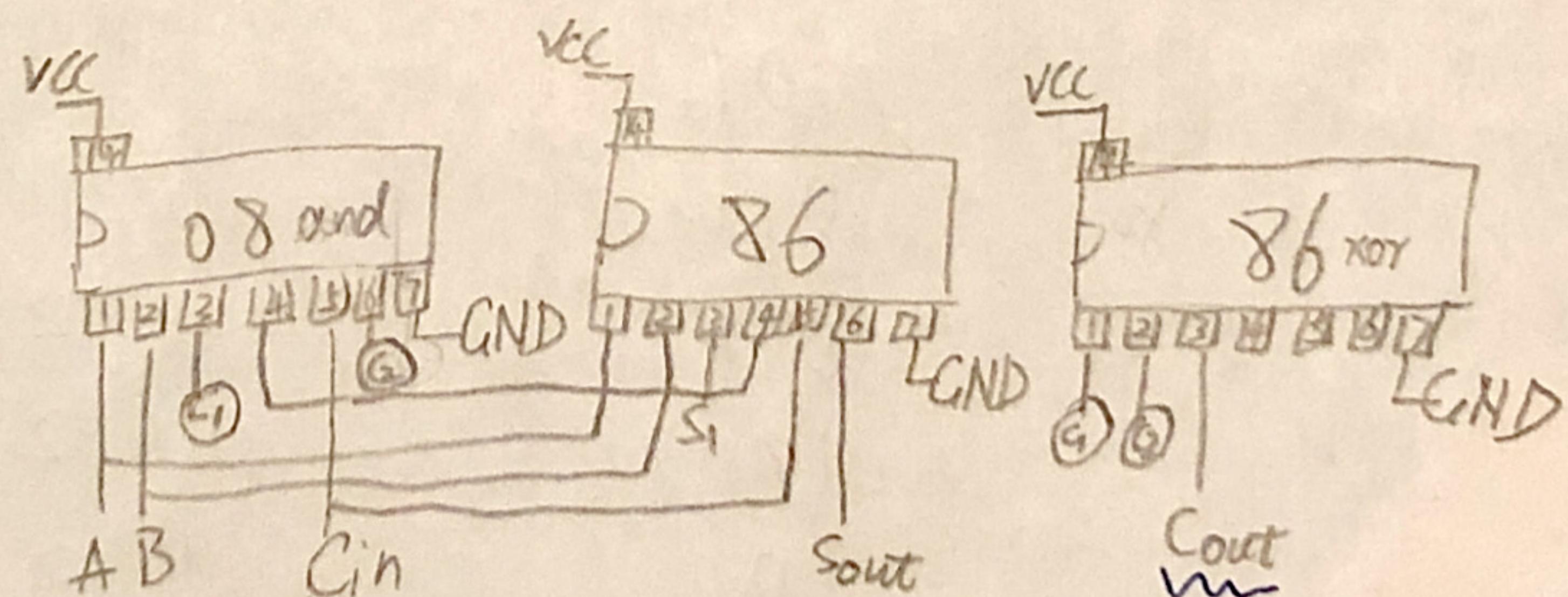


Circuit Demonstration Page

Half adder schematicHalf adder wiring diagramHalf adder: AKQFull adder schematicFull adder wiring diagramFull adder: AKQAKQ

2-bit adder: _____