

# ELC 2137 Lab 02: Transistor Logic Gates

Yiting Wang

September 10, 2020

## Summary

Gates are made up of switches (on/off). How you connect them determines the type of gate; Transistors are voltage-controlled switches, so we can hook gates together.

## Q&A

1. What logic operation does it implement? it's AND gate

## Results

Table 1: Logic/truth table for the Final gate

A	B	LED
0	0	0
0	1	0
1	0	0
1	1	1



Figure 1: This is the Circuit Demonstration Page 1.

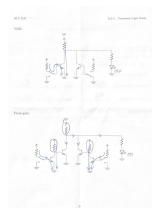


Figure 2: This is the Circuit Demonstration Page 2.

## Code

Table 2: Logic/truth table for the Final gate

A	B	LED
0	0	0
0	1	0
1	0	0
1	1	1

## Circuit Demonstration Page

Student names: Yitao Wang \_\_\_\_\_  
 \_\_\_\_\_

### Instructor Initials

Pushbutton "Or Gate" KEQ

Transistor Not gate KEQ

Transistor Nor gate KEQ

Transistor unknown gate BSS

### Diagrams

On each of the circuits below, draw the current paths and note whether each switch, transistor, and LED is ON or OFF.

Inverter:


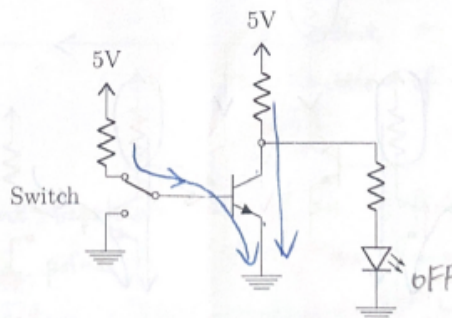


Figure 3: This is the Circuit Demonstration Page 1.

NOR:

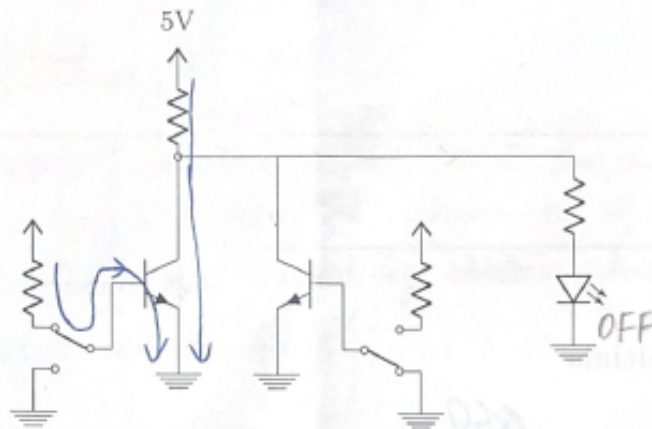

Final gate:

